



UNITED INTERNATIONAL UNIVERSITY (UIU)

Dept. of Computer Science & Engineering

Trimester: Summer 2023

Final Exam

Course No: CSE 1326

Title: DLD LAB

Section: D



Time: 20 minutes

Marks: 25

Name	ID
------	----



(Just Put a single tick mark on the right option in the MCQ Question, if you double tick in any MCQ Question, you will get zero in that question) [MCQ: 6×2.5=15 marks]

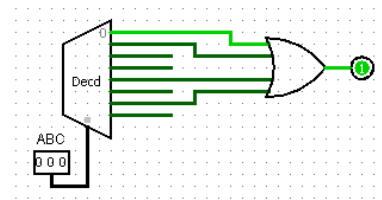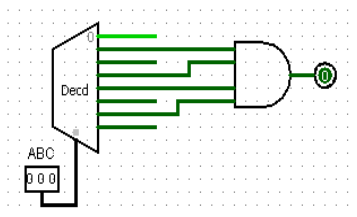- 1). If output of X-NOR gate is 1, what are the inputs?
 - a) $A = 0, B = 1$
 - b) $A = 1, B = 0$
 - c) $A' = 0, B = 0$
 - d) **$A = 0, B = 0$**
- 2). For a sequence recognizer to detect a bit pattern of “0010”, the states are s0, s1, s2 & s3. If the value of input x = 0 for state s2, what will be output and next state?
 - a) output 0, state: s3
 - b) output 1, state: s3
 - c) **output 0, state: s2**
 - d) output 1, state: s2
- 3). What are the inputs of a 4-bit full adder if the carry-in is ‘1’ and output is ‘10010’?
 - a) 1011 & 0111
 - b) 1010 & 1000
 - c) 1111 & 1110
 - d) **0110 & 1011**
- 4). Suppose, you’re designing a data transmission system where you need to choose between 8 different data sources based on a control signal. Which digital component would allow you to select one of the 8 data sources with how much selection bit?
 - a) **Multiplexer, number of selection bit: 3**
 - b) Decoder, number of selection bit:3
 - c) Multiplexer, number of selection bit: 2
 - d) Decoder, number of selection bit:2
- 5). What will be logic diagram for $F = m_2 + m_3 + m_5 + m_7$ by using 3-to-8 line active low decoder? (**Right answer: C**)
 - a)
 - b)



c)

d)

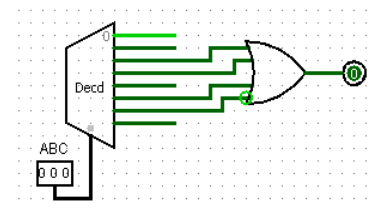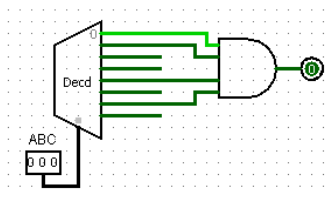

- 6). What is the simplification for the following Boolean expression, $F = AB + A'B + AB'$.
 - a) **$A + B$**
 - b) $AB' + B$
 - c) $A'B + A$

d) $A' + B$

[Written: 2×5=10 marks]

7) Draw the state diagram for a sequence recognizer that can detect the pattern 010 considering the overlapping pattern.

8) Draw the circuit diagram of a counter using negative edge D Flipflop that has the following sequence: 1, 2, 3, 4,31, 0, 1, 2,